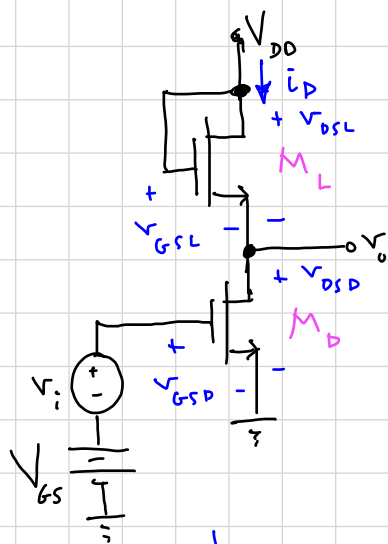


Lecture # 21





Single- and multi-stage Amplifier IC's

- Resistors are less practical for IC's than MOSFETs
- Need to achieve amplifiers from all-MOSFET IC's
- Can do this using inverter-style circuits but with ac input.

NMOS Amplifier with Enhancement Load



Small-signal equiv. circuit

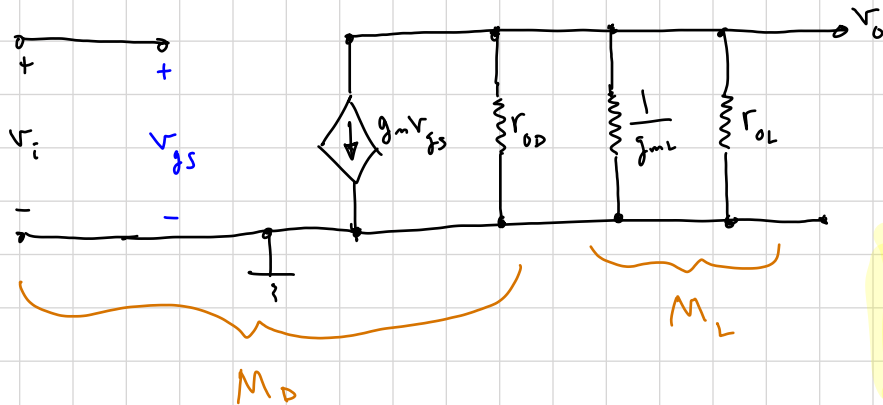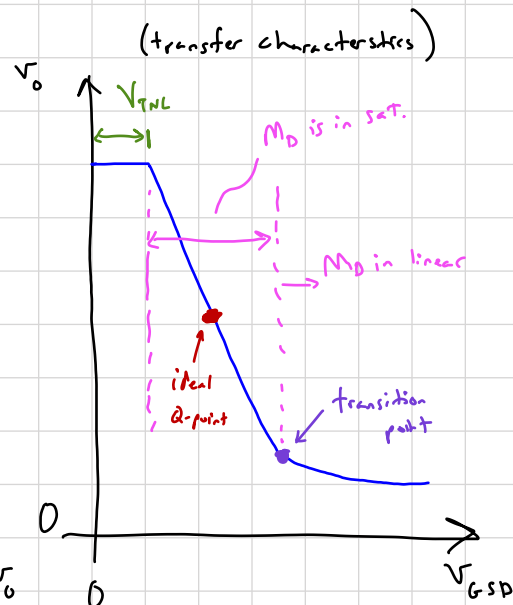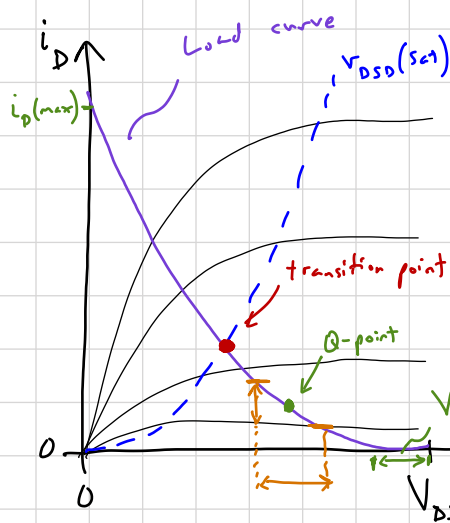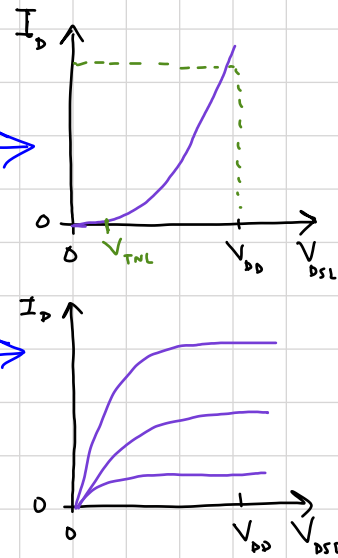


$$A_v = \frac{v_o}{v_i} = -g_m \left(r_{op} \parallel \frac{1}{g_{mL}} \parallel r_{oL} \right)$$

→ generally: $\frac{1}{g_{mL}} \ll r_{oL}$, $\frac{1}{g_{mD}} \ll r_{oD}$

$$A_v = -\frac{g_{mD}}{g_{mL}} = -\sqrt{\frac{K_{nD}}{K_{nL}}} = -\sqrt{\frac{\left(\frac{W}{L}\right)_D}{\left(\frac{W}{L}\right)_L}}$$





CMOS Common-Source Amplifier

→ CMOS Amplifiers are the most relevant

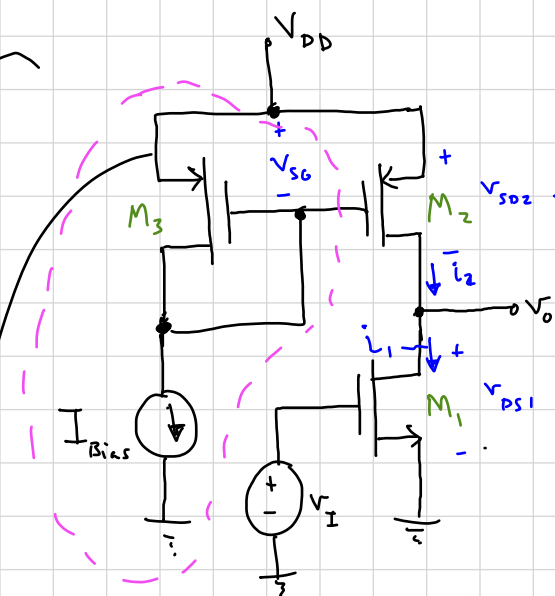



Bias M_2 with this to enable more precise setting of Q-point & causes $i_2 = I_{Bias}$ (see Fig. 3.49)

Small-sig. equiv. circuit

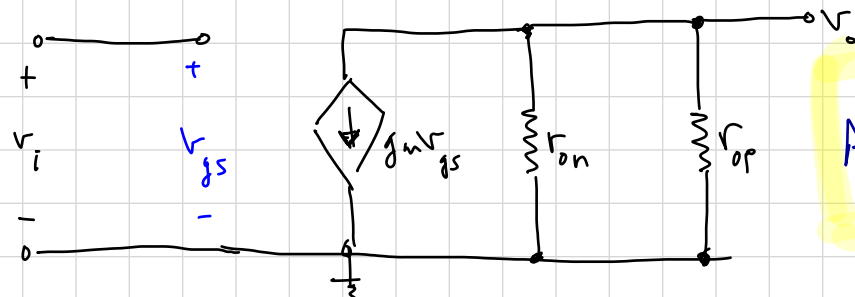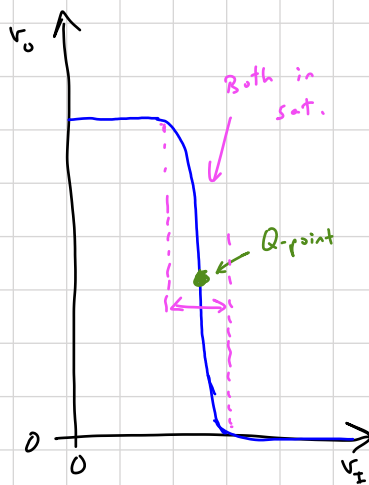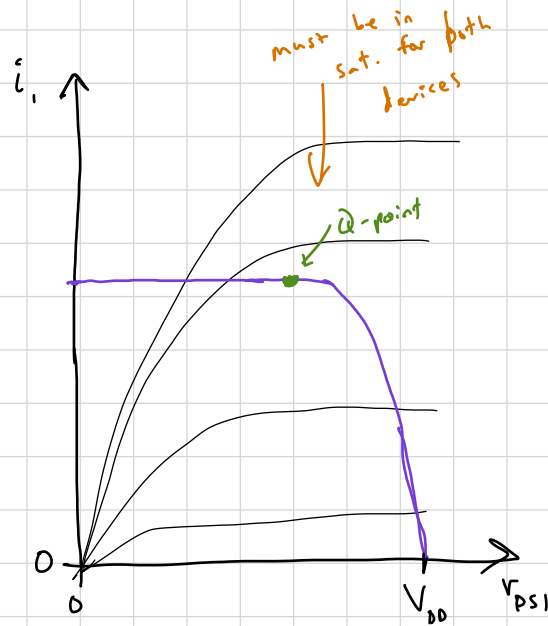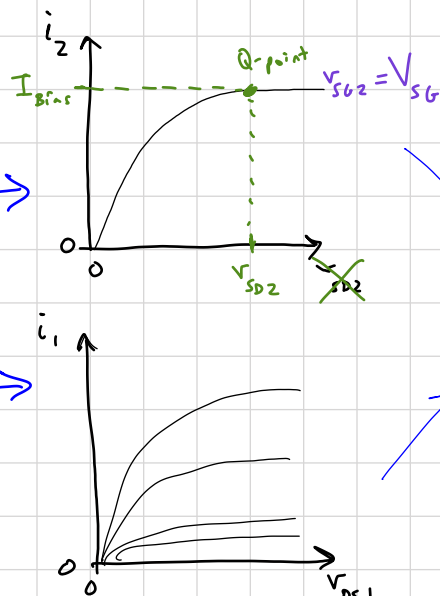

$$A_v = \frac{v_o}{v_i} = -g_m (r_{on} \parallel r_{op})$$

CMOS Common-Gate Amplifier

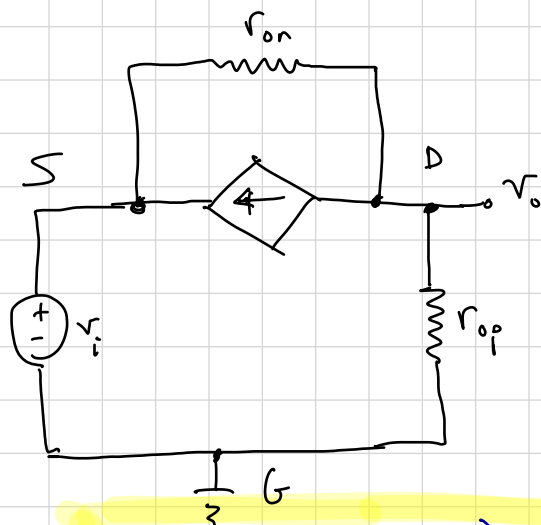
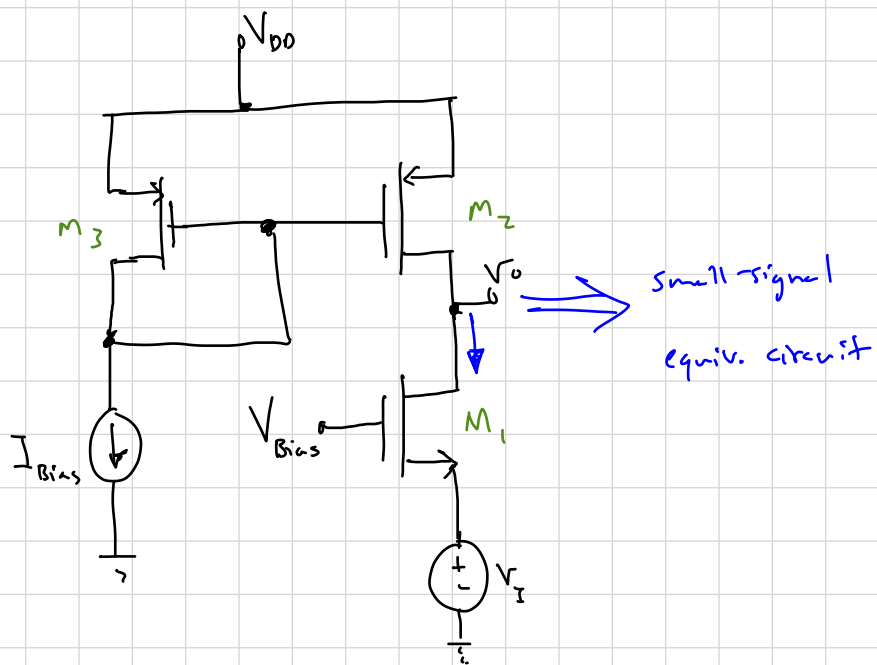


$$A_v = \frac{\left(g_{m1} + \frac{1}{r_{on}}\right)}{\left(\frac{1}{r_{op}} + \frac{1}{r_{on}}\right)}$$

Multi-stage Amplifiers

- single-stage amplifiers often can't get the job done
- cascade them together:

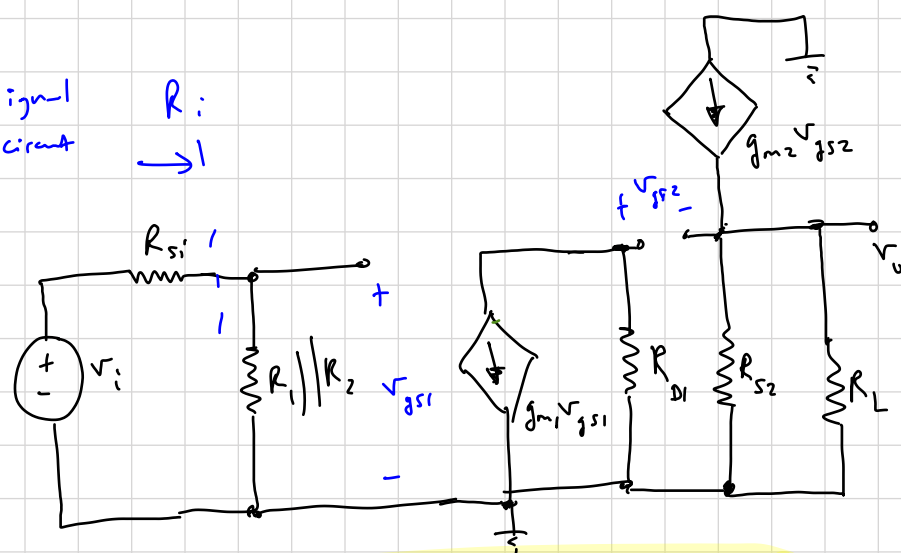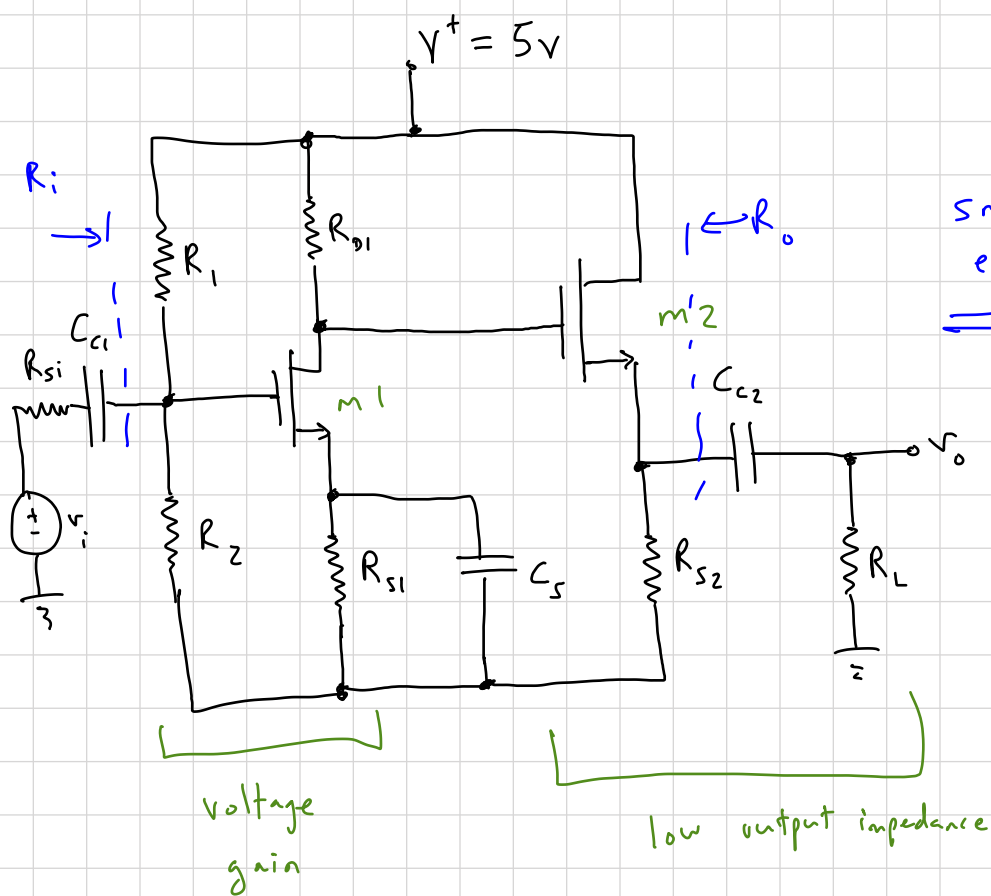EX: Common-Source followed by common-drain



$$A_v = \frac{-g_{m1} g_{m2} R_{D1} (R_{S2} \parallel R_L)}{1 + g_{m2} (R_{S2} \parallel R_L)} \left(\frac{R_i}{R_i + R_{S1}} \right)$$