

# Lecture #11

## pn junction transients: large-signal analysis

→ Small-signal admittance: (wrapping up from last lecture)


$$Y = g_d + j\omega C_d = \frac{I_{DQ}}{V_t} = \frac{1}{V_t} (I_{p0} + I_{n0})$$

Where the diffusion cap:  $C_d = \left( \frac{1}{2V_t} \right) (I_{p0} \tau_{p0} + I_{n0} \tau_{n0})$

the DC currents
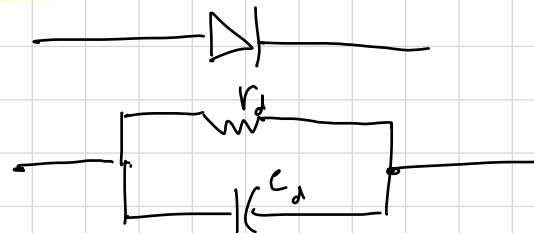
### Equivalent Circuit

- In the ideal case, just consider  $r_d$  and  $C_d$ :




- Complete circuit includes  $C_j$  and series resistance,  $r_s$

Voltage across junction:  $V_a$

Total applied voltage:  $V_{app}$


$$V_{app} = V_a + r_s I_0$$

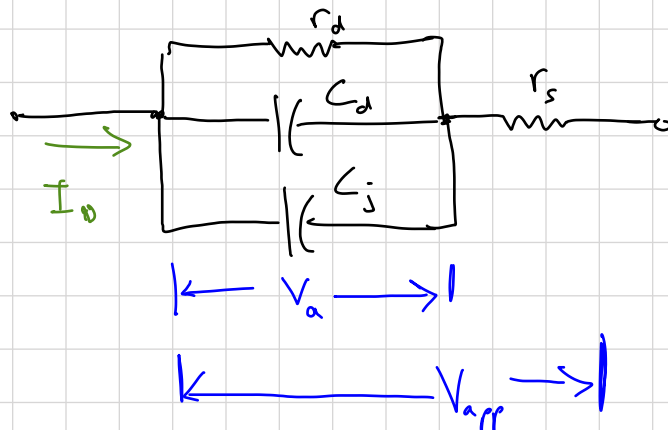


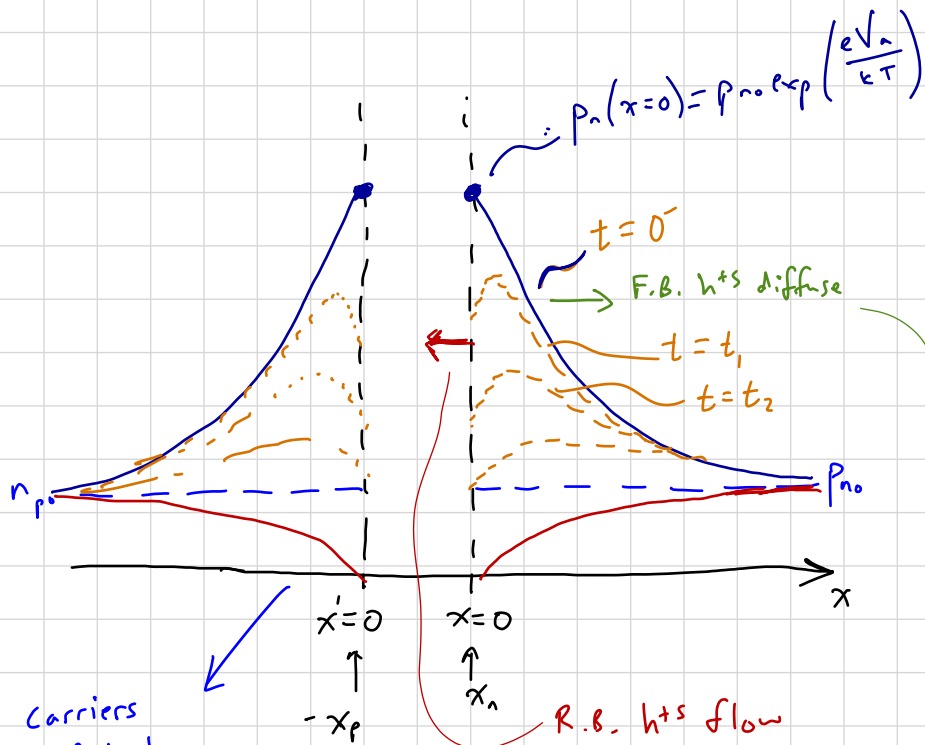
### Diode Transients

→ In circuit applications, the "speed" of a pn junction switching is important.

- switching from forward to reverse-bias
- Voltage is abruptly changed from forward to reverse-bias at  $t=0$
- Junction capacitances do not allow junction voltage to change instantly (gradual discharge)



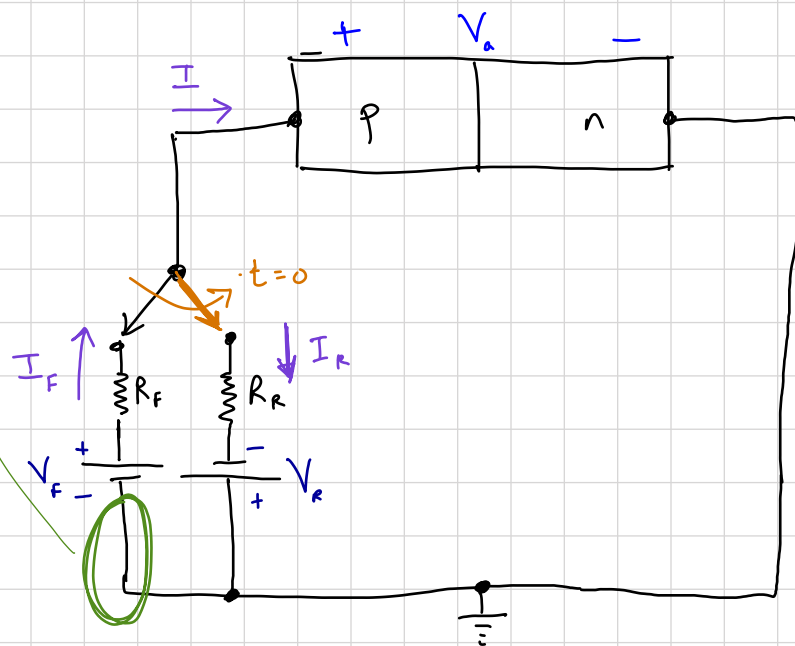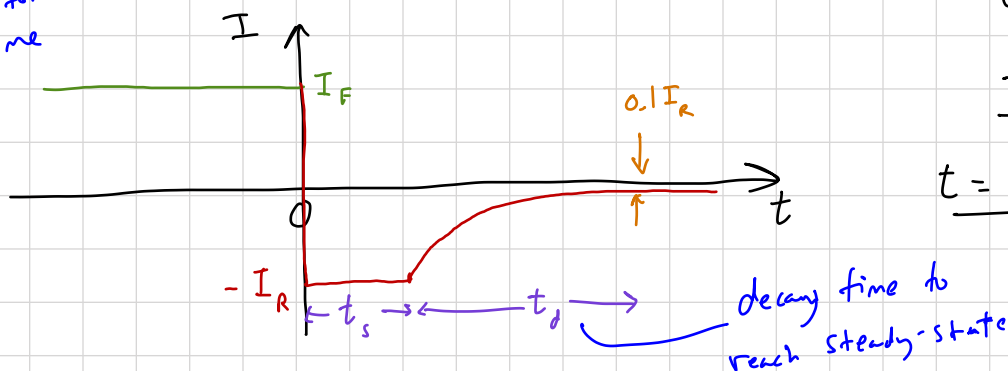carriers are effectively "stored" for some time



$$t < 0: I = I_F = \frac{V_F - V_a}{R_F}$$

$$t > 0: I = -I_R \approx -\frac{V_R}{R_R}$$

$$t = t_s: t_s \approx \tau_{p0} \ln\left(1 + \frac{I_F}{I_R}\right)$$

for one-sided junction (p+n)




# pn diode circuits large-signal (DC) analysis

must consider  
non-linearity

can assume  
linearity



★ Look in textbook for difference between large-signal and small-signal

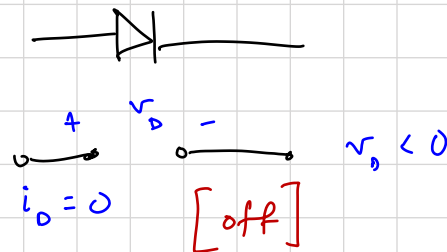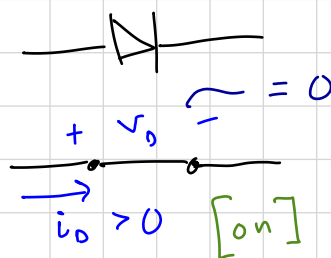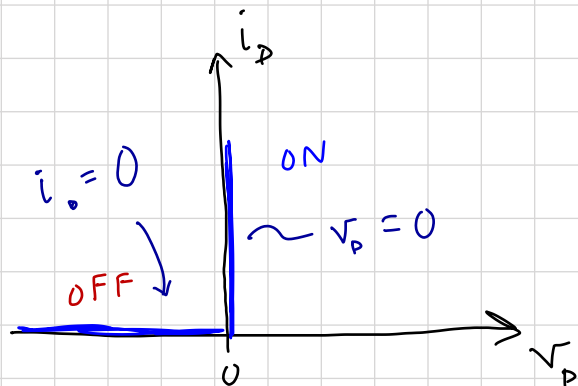An "Ideal diode" (different than the ideal diode eqn.) as a circuit element would do the following:



★ This allows conceptualization of how a diode circuit functions but need more work for actual analysis:

Ex: Half-wave rectifier

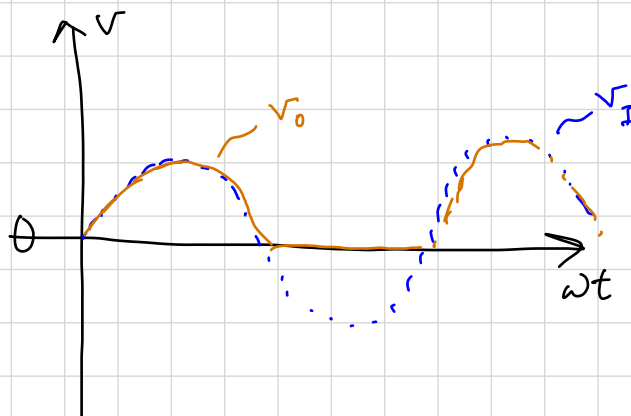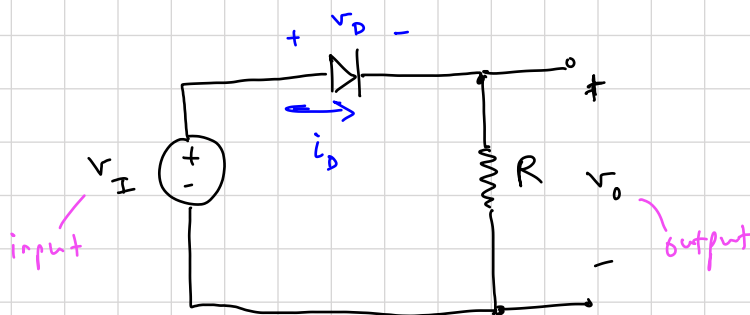


For analyzing diode circuits with large signals (or DC), there are options:

First, recall Kirchhoff's voltage & current laws (KVL, KCL):

KVL

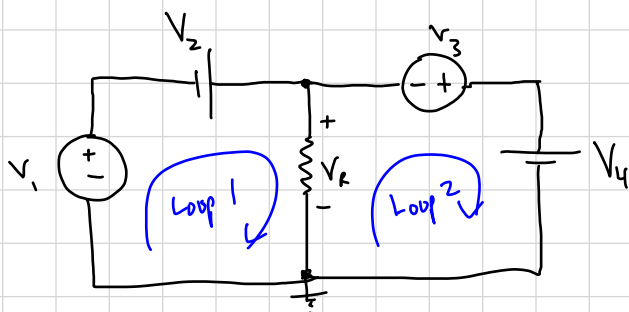Sum of all voltages around a loop is zero




$$\text{Loop 1: } -v_1 - v_2 + v_R = 0$$

$$\text{Loop 2: } -v_R - v_3 + v_4 = 0$$


KCL

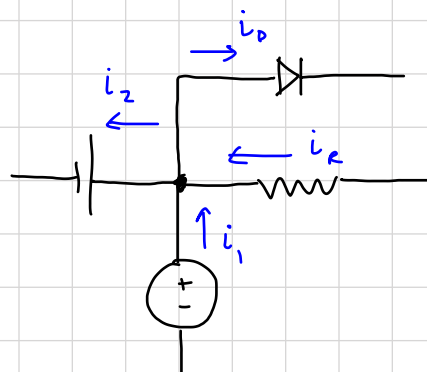current entering a junction/node is equal to current leaving that junction




$$i_1 + i_R = i_2 + i_D$$
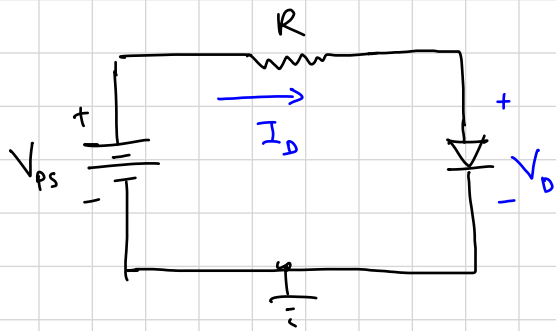
# Techniques for analyzing large-signal diode circuits:



piecewise linear =

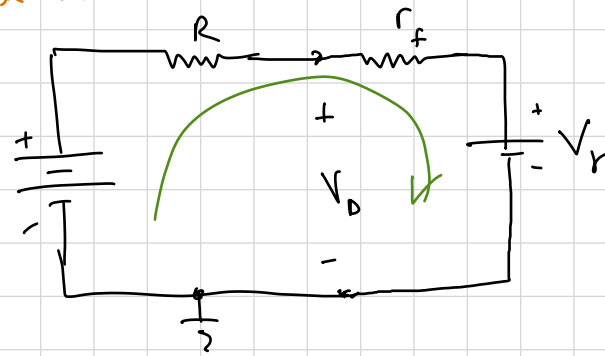

## Iteration

KVL:

$$V_{ps} = I_D R + V_D$$

$$I_D = \frac{V_{ps}}{R} - \frac{V_D}{R}$$

Recall ideal diode eqn.:

$$I_D = I_s \left[ \exp\left(\frac{V_D}{V_t}\right) - 1 \right]$$

$$V_{ps} = I_s R \left[ \exp\left(\frac{V_D}{V_t}\right) - 1 \right] + V_D$$

→ Typically given:  $V_{ps}, I_s, R$

→ Find  $V_D$  and then  $I_D$  by trial and error (iteration)

$I_s$  must be given


## Graphical Analysis

$$I_D = \frac{V_{ps} - V_D}{R}$$

→ linear relationship between  $V_D$  and  $I_D$  for a given power supply voltage

LOAD LINE

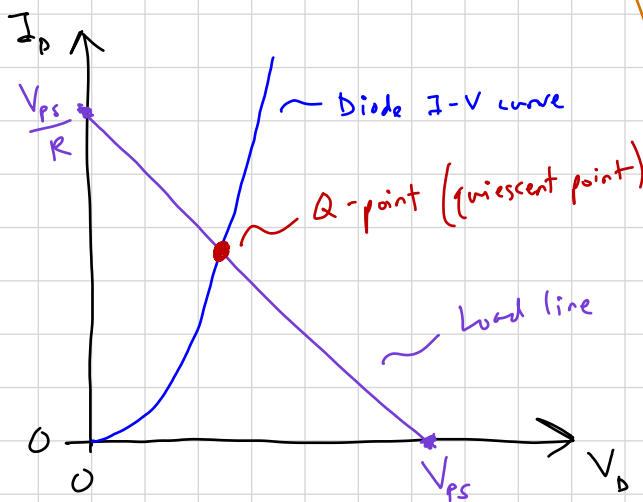
→ relationship between  $I_D$  and  $V_D$  for a given circuit





→ extract  $I_D, V_D$  from the Q-point
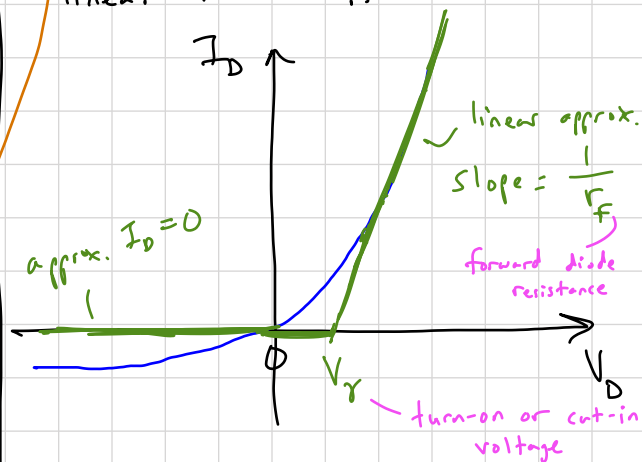
## Piecewise Linear Model

→ approx. diode's nonlinear I-V using linear relationships




Diode looks like:

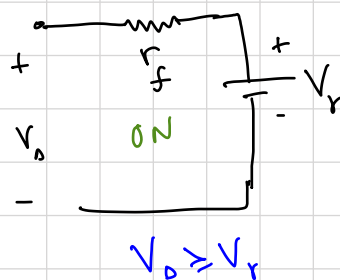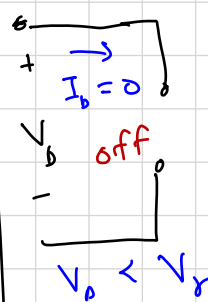

★ must be given  $V_r$  and  $r_f$

Common standard assumptions { OR assume:  $V_r = 0.7V$  and  $r_f = 0$

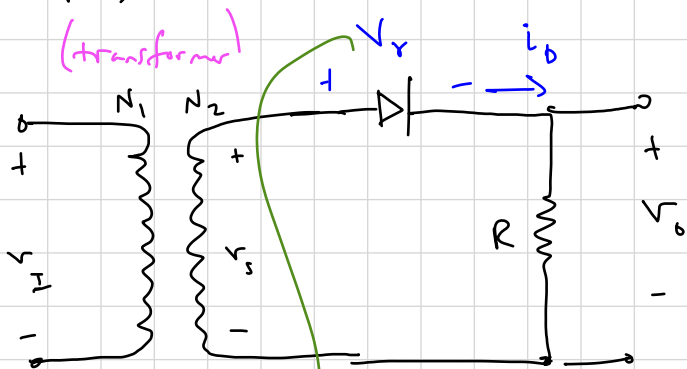Apply this analysis to the half-wave rectifier:



use piecewise linear model assuming  $V_r = 0.7V$  and  $r_f = 0$  ( $r_f \ll R$ )

KVL:

$$V_s = V_r + i_D R$$

$$i_D = \frac{V_s - V_r}{R}$$

AND

$$V_D = i_D R = V_s - V_r$$

$$KVL: I_D = \frac{V_{ps} - V_r}{R + r_f}$$

$$V_D = V_r + I_D r_f$$

★ NOTE: None of these are 'universal' equations, but come from analyzing the given circuit!