

Homework #11

Operational Amplifiers – *100 points*

DUE @ Beginning of Class: Tuesday, December 5

- 1) E-Book, problem 9.2 (*12 points*)
- 2) E-Book, problem 9.6 (*10 points*)
- 3) E-Book, problem 9.7 (*14 points*)
- 4) E-Book, problem 9.19 (*14 points*)
- 5) E-Book, problem 9.25 (*20 points*)
- 6) E-Book, problem D9.35 (*10 points*)
- 7) E-Book, problem D9.60 (*20 points*)

1) E-Book, problem 9.2 (12 points)

9.2 The op-amp in the circuit shown in Figure P9.2 is ideal except it has a finite open-loop gain. (a) If $A_{od} = 10^4$ and $v_O = -2$ V, determine v_I . (b) If $v_I = 2$ V and $v_O = 1$ V, determine A_{od} .

a) Since the input is on (2):

$$v_z = \frac{v_o}{A_{od}} = \frac{-2 \text{ V}}{10^4} = 2 \times 10^{-4} \text{ V}$$

voltage divider:

$$v_z = \left(\frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 2000 \text{ k}\Omega} \right) v_I$$

$$2 \times 10^{-4} \text{ V} = \left(\frac{1}{2001} \text{ k}\Omega \right) v_I \Rightarrow v_I = -0.4 \text{ V} \quad \mathbf{8}$$

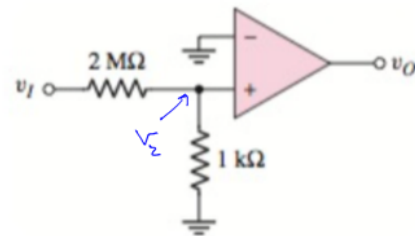


Figure P9.2

$$b) v_z = \left(\frac{1}{2001} \text{ k}\Omega \right) v_I = 0.9995 \times 10^{-3} \text{ V}$$

$$v_o = 1 \text{ V} = A_{od} v_z = A_{od} (0.9995 \times 10^{-3} \text{ V}) \Rightarrow A_{od} = 1000.5 \quad \mathbf{4}$$

2) E-Book, problem 9.6 (10 points)

9.6 Assume the op-amps in Figure P9.6 are ideal. Find the voltage gain $A_v = v_O/v_I$ and the input resistance R_i of each circuit.

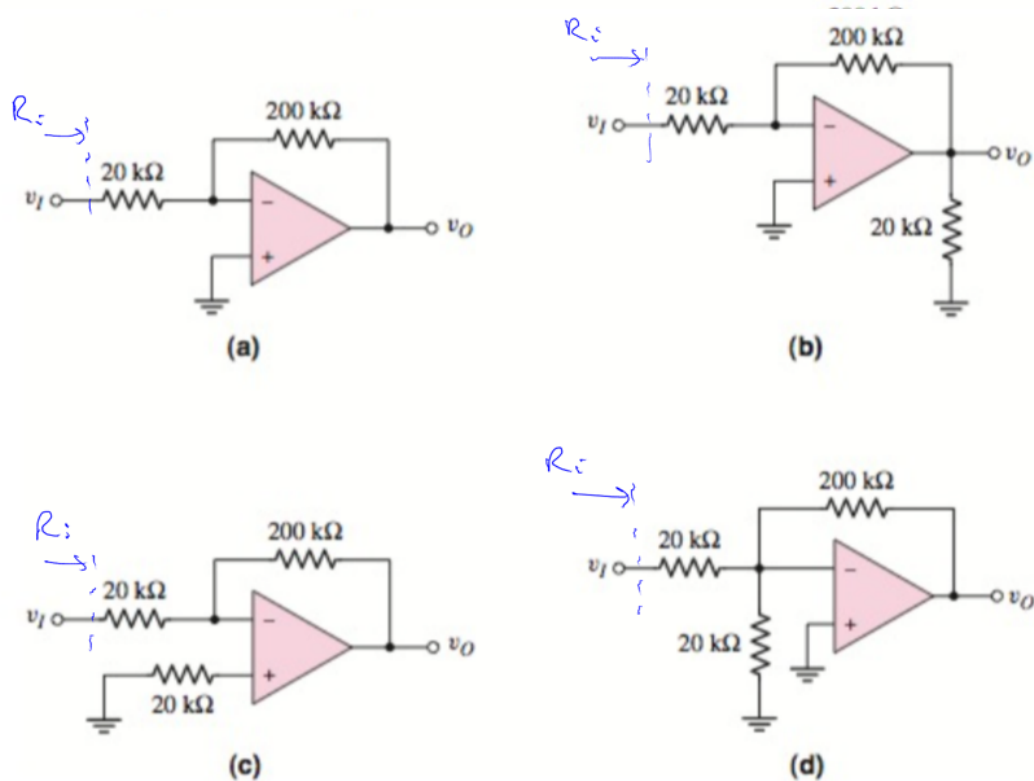


Figure P9.6

Each one of these is a negative feedback, inverting op-amp having the same $R_i = 20\text{ k}\Omega$ and gain, $A_v = -\frac{R_2}{R_1} = -\frac{200\text{ k}\Omega}{20\text{ k}\Omega} = -10$

2 pts for each part


3) E-Book, problem 9.7 (14 points)

9.7 Consider an ideal inverting op-amp with $R_2 = 100\text{ k}\Omega$ and $R_1 = 10\text{ k}\Omega$.

(a) Determine the ideal voltage gain and input resistance R_i . (b) Repeat part (a) for a second $100\text{ k}\Omega$ resistor connected in parallel with R_2 . (c) Repeat part (a) for a second $10\text{ k}\Omega$ resistance connected in series with R_1 .


a) $A_v = -\frac{R_2}{R_1} = -\frac{100\text{ k}\Omega}{10\text{ k}\Omega} = -10$ 2

$R_i = R_1 = 10\text{ k}\Omega$ 2

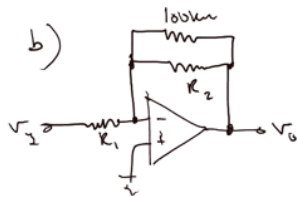

$A_v = -\frac{R_2 \parallel 100\text{ k}\Omega}{R_1} = -\frac{100\text{ k}\Omega \parallel 100\text{ k}\Omega}{10\text{ k}\Omega} = -5$ 3

$R_i = R_1 = 10\text{ k}\Omega$ 3

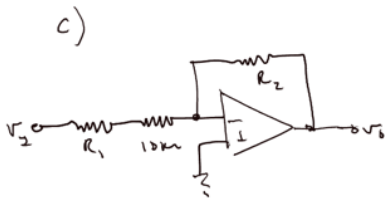

$A_v = -\frac{R_2}{R_1 + 10\text{ k}\Omega} = -\frac{100\text{ k}\Omega}{10\text{ k}\Omega + 10\text{ k}\Omega} = -5$ 2

$R_i = 10\text{ k}\Omega + 10\text{ k}\Omega = 20\text{ k}\Omega$ 2

4) E-Book, problem 9.19 (14 points)

9.19 Consider the circuit shown in Figure P9.19. (a) Determine the ideal output voltage v_O if $v_I = -0.40$ V. (b) Determine the actual output voltage if the open-loop gain of the op-amp is $A_{od} = 5 \times 10^3$. (c) Determine the required value of A_{od} in order that the actual voltage gain be within 0.2 percent of the ideal value.

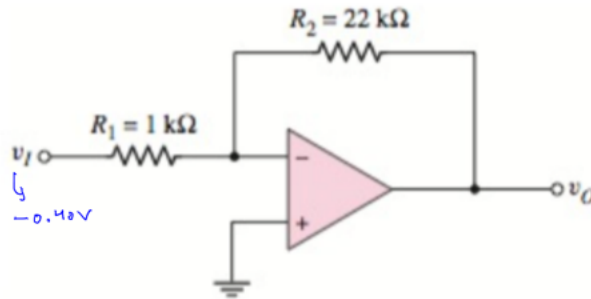


Figure P9.19

a)
$$v_o = -\frac{R_2}{R_1} v_i = -\left(\frac{22\text{ k}\Omega}{1\text{ k}\Omega}\right)(-0.40\text{ V}) = 8.8\text{ V}$$
 4

b) Since finite open-loop gain:

$$A_v = -\frac{R_2}{R_1} \left(\frac{1}{1 + \frac{1}{A_{od}} \left(1 + \frac{R_2}{R_1} \right)} \right) = -(22) \left(\frac{1}{1 + \frac{1}{5 \times 10^3} (1 + 22)} \right) = -21.9$$
 4

c) within 0.2% of ideal would be:

$$A_v = -\left(\frac{22\text{ k}\Omega}{1\text{ k}\Omega}\right)(0.998) = -21.956$$

$$-21.956 = -(22) \left(\frac{1}{1 + \frac{1}{A_{od}} (23)} \right) \Rightarrow A_{od} = 1.148 \times 10^4$$
 6

5) E-Book, problem 9.25 (20 points)

9.25 For the op-amp circuit shown in Figure P9.25, determine the gain $A_v = v_O/v_I$. Compare this result to the gain of the circuit shown in Figure 9.12, assuming all resistor values are equal.

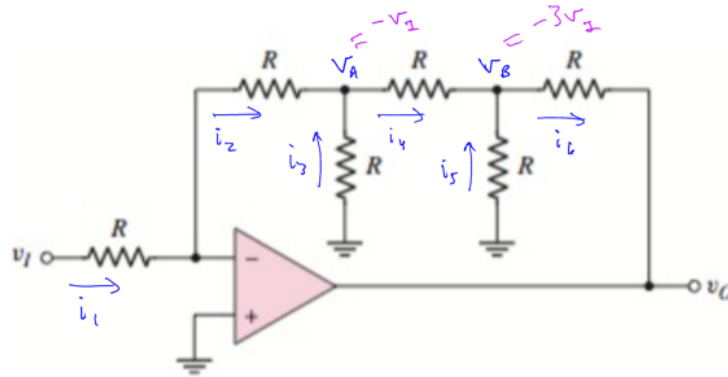


Figure P9.25

$$i_1 = \frac{v_I}{R} = i_2$$

$$v_A = -i_2 R = -\left(\frac{v_I}{R}\right)R = -v_I$$

$$i_3 = -\frac{v_A}{R} = \frac{v_I}{R}$$

$$i_4 = i_2 + i_3 = -\frac{v_I}{R} - \frac{v_I}{R} = -\frac{2v_I}{R} = \frac{2v_I}{R} \quad 6$$

$$v_B = v_A - i_4 R = -v_I - \left(\frac{2v_I}{R}\right)R = -3v_I$$

$$i_5 = -\frac{v_B}{R} = -\frac{(-3v_I)}{R} = \frac{3v_I}{R}$$

$$i_6 = i_4 + i_5 = \frac{2v_I}{R} + \frac{3v_I}{R} = \frac{5v_I}{R}$$


$$v_O = v_B - i_6 R = -3v_I - \left(\frac{5v_I}{R}\right)R \Rightarrow \frac{v_O}{v_I} = A_v = -8 \quad 8$$

From Fig. 9.12, $A_v = -3$, so the additional T-branch increased A_v .

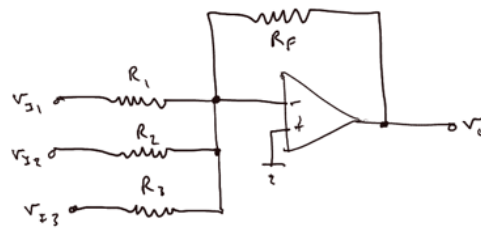6) E-Book, problem D9.35 (10 points)

D9.35 (a) Design an ideal summing op-amp circuit to provide an output voltage of $v_O = -2[(v_{I1}/4) + 2v_{I2} + v_{I3}]$. The largest resistor value is to be 250 k Ω .(b) Using the results of part (a), determine the range in output voltage and the maximum current in R_F if the input voltages are in the ranges $-2 \leq v_{I1} \leq +2$ V, $0 \leq v_{I2} \leq 0.5$ V, and $-1 \leq v_{I3} \leq 0$ V.

$$\begin{aligned} a) \quad v_O &= -\left(\frac{R_F}{R_1} v_{I1} + \frac{R_F}{R_2} v_{I2} + \frac{R_F}{R_3} v_{I3}\right) \\ &= -2\left(\frac{v_{I1}}{4} + 2v_{I2} + v_{I3}\right) \\ &= -\frac{1}{2} v_{I1} - 4v_{I2} - 2v_{I3} \end{aligned}$$



$$\Rightarrow \frac{R_F}{R_1} = \frac{1}{2}, \quad \frac{R_F}{R_2} = 4, \quad \frac{R_F}{R_3} = 2$$

$$R_1 = 250 \text{ k}\Omega, \quad R_F = 125 \text{ k}\Omega, \quad R_2 = 31.25 \text{ k}\Omega, \quad R_3 = 62.5 \text{ k}\Omega$$

2 each

$$b) \quad \text{For } v_{I1} = -2 \text{ V}, \quad v_{I2} = 0 \text{ V}, \quad v_{I3} = -1 \text{ V}$$

$$v_O = -\frac{1}{2}(-2) - 4(0) - 2(-1) = 3 \text{ V}$$

$$\text{For } v_{I1} = 2 \text{ V}, \quad v_{I2} = 0.5 \text{ V}, \quad v_{I3} = 0$$


$$v_O = -\frac{1}{2}(2) - 4(0.5) - 2(0) = -3 \text{ V}$$

$$\text{Then: } -3 \text{ V} \leq v_O \leq 3 \text{ V} \quad \mathbf{1}$$

$$|i_F|_{\text{max}} = \frac{|v_O|_{\text{max}}}{R_F} = \frac{3 \text{ V}}{125 \text{ k}\Omega} = 24 \mu\text{A} \quad \mathbf{1}$$

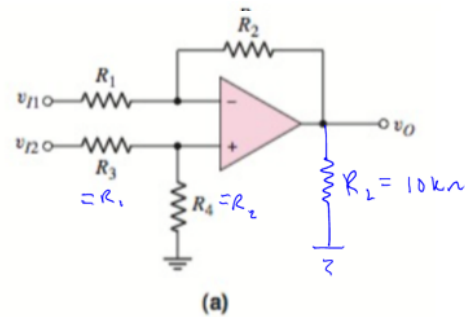7) E-Book, problem D9.60 (20 points)

D9.60 Consider the op-amp difference amplifier in Figure 9.24(a). Let $R_1 = R_3$ and $R_2 = R_4$. A load resistor $R_L = 10\text{ k}\Omega$ is connected from the output terminal to ground. (a) Design the circuit such that the difference voltage gain is $A_d = 15$ and the minimum difference input resistance is $30\text{ k}\Omega$. (b) If the load current is $i_L = 0.25\text{ mA}$, what is the differential input voltage ($v_{I2} - v_{I1}$)? (c) If $v_{I1} = 1.5\text{ V}$ and $v_{I2} = 1.2\text{ V}$, determine i_L . (d) If $i_L = 0.5\text{ mA}$ when $v_{I2} = 2.0\text{ V}$, determine v_{I1} .



a) $A_d = 15$, $R_{id} = 30\text{ k}\Omega$

$$R_{id} = R_1 + R_3 = 30\text{ k}\Omega$$

$$\rightarrow R_1 = R_3 = 15\text{ k}\Omega \quad 4$$

$$\frac{R_2}{R_1} = \frac{R_4}{R_3} = 15 \Rightarrow R_2 = R_4 = 225\text{ k}\Omega \quad 4$$

b) $v_o = i_L R_L = (0.25\text{ mA})(10\text{ k}\Omega) = 2.5\text{ V} = \frac{R_2}{R_1} (v_{I2} - v_{I1})$

$$v_{I2} - v_{I1} = \frac{2.5}{15} = 0.167\text{ V} \quad 4$$

c) $v_o = \frac{R_2}{R_1} (v_{I2} - v_{I1}) = (15)(1.2 - 1.5) = -4.5\text{ V}$

$$i_L = \frac{v_o}{R_L} = \frac{-4.5\text{ V}}{10\text{ k}\Omega} = -0.45\text{ mA} \quad 4$$

d) $v_o = (0.5)(10\text{ k}\Omega) = 5\text{ V}$

$$v_{I2} - v_{I1} = \frac{5\text{ V}}{15} = 0.333\text{ V}$$

$$v_{I1} = 2 - 0.333\text{ V} = 1.667\text{ V} \quad 4$$