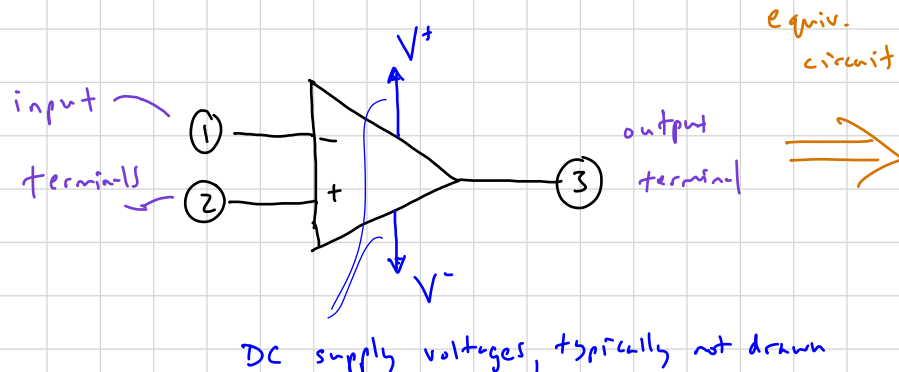


# Lecture # 22


## The Operational Amplifier (Op-Amp)

### Intro to Op-Amp

- Integrated circuit that amplifies the difference between two input voltages, producing a single output.
- Function / use changes depending on how it is connected and what it is connected to.



equiv. circuit

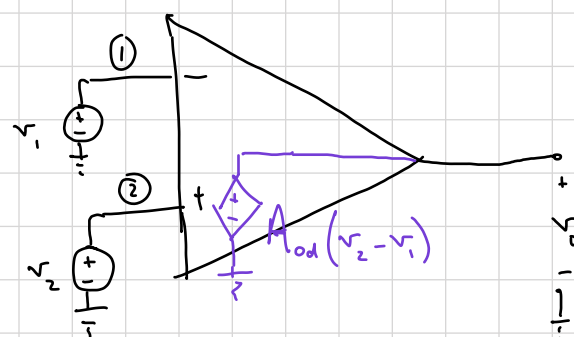

★ No coupling capacitors, so inputs can be pure DC or AC voltages

$A_{ol} \equiv$  open-loop differential voltage gain


①  $\equiv$  inverting input terminal

②  $\equiv$  noninverting input terminal


### Ideal Op-Amp with "Negative Feedback"

Ideal op-amp means:

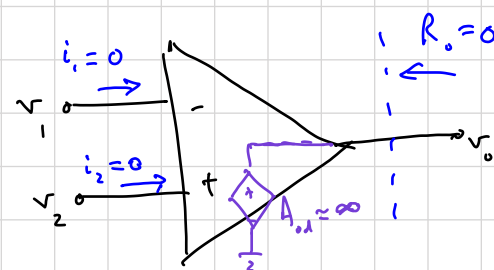- 1)  $A_{ol}$  is  $\infty$
- 2) Differential input voltage,  $v_2 - v_1 = 0$
- 3) Input resistances  $= \infty$ ,  $i_1 = i_2 = 0$
- 4) Output resistance,  $R_o = 0 \Rightarrow v_o$  connected directly to  $A_{ol}(v_2 - v_1)$  and independent of any load on output.



### Basic Inverting Op-Amp

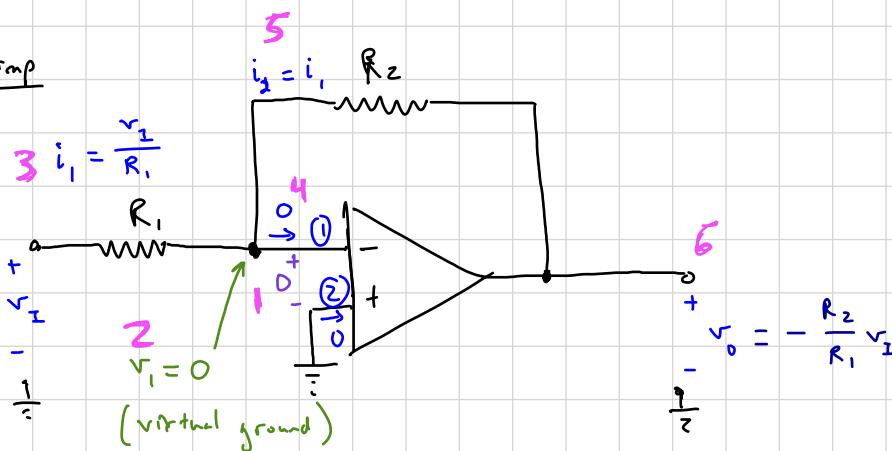

What will the closed-loop voltage gain be?

$$A_v = \frac{v_o}{v_i}$$

• minus sign means op-amp leads to signal inversion

•  $A_v$  depends entirely on external passive components

- can design very accurate  $A_v$
- stable and predictable!
- works for AC or DC inputs!

$$1 - v_2 - v_1 = \frac{v_o}{A_{ol}} = 0$$

$$2 - v_1 = v_2 \equiv v_i \text{ is "virtual ground"}$$

$$3 - i_1 = \frac{v_i - v_1}{R_1} = \frac{v_i}{R_1}$$


$$4 - \infty \text{ input impedance of op-amp}$$

$$5/6 - v_o = v_1 - i_2 R_2 = 0 - \left(\frac{v_i}{R_1}\right) R_2 \therefore A_v = -\frac{R_2}{R_1}$$

★ Has zero voltage but is not physically connected to ground.
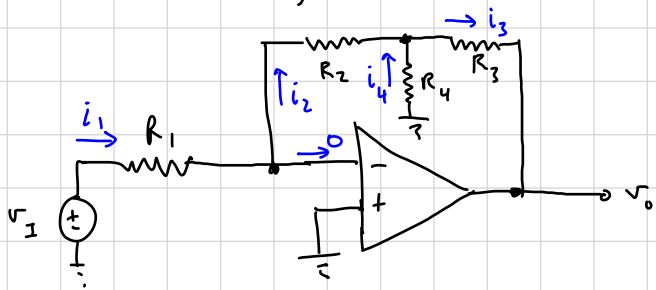
## • Op-Amp with a T-network

→ Basic inverting config is limited by difficulty of implementing very large resistors for  $R_2$




$$A_v = -\frac{R_2}{R_1} \left( 1 + \frac{R_3}{R_4} + \frac{R_3}{R_2} \right)$$

## • Effect of finite gain

→ Key assumption thus far for "ideal op-amp" is  $A_{od} = \infty$

→ What if it does not?

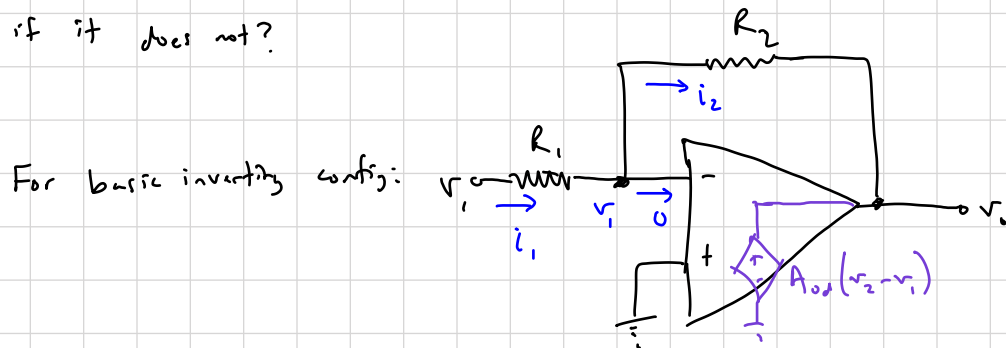


$$i_1 = \frac{v_i - v_1}{R_1} = i_2 = \frac{v_1 - v_o}{R_2}$$

$$v_o = -A_{od} v_1 \rightarrow v_1 = -\frac{v_o}{A_{od}}$$

add this eqn to  
and solve for  $v_o/v_i$ :

$$A_v = -\frac{R_2}{R_1} \left( \frac{1}{1 + \frac{1}{A_{od}} \left( 1 + \frac{R_2}{R_1} \right)} \right)$$

## • Summing Amplifier

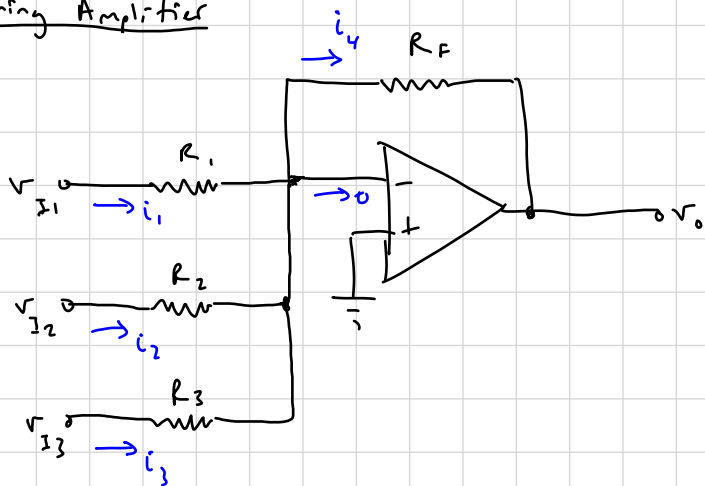

★ Can use superposition to analyze by summing up the different input contributions (set others to zero, solve, etc.)


result:

$$v_o = -\frac{R_F}{R_1} (v_{i1} + v_{i2} + v_{i3})$$

if  $R_1 = R_2 = R_3$
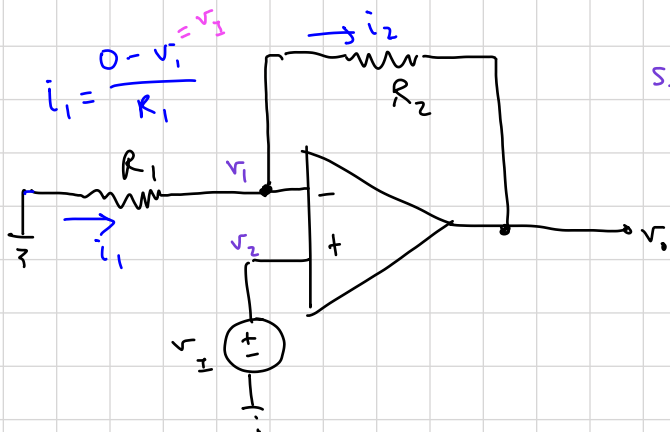
## • Non-inverting Amplifier

→ apply input signal to non-inverting terminal (2)




Still have  $v_1 = v_2$ , now a "virtual short"

$$A_v = 1 + \frac{R_2}{R_1}$$

★ in-phase output with input

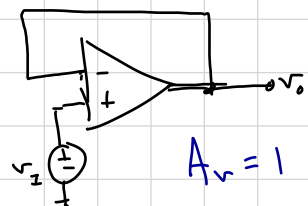used mostly as "voltage-follower"  
or impedance transformer:



See book example