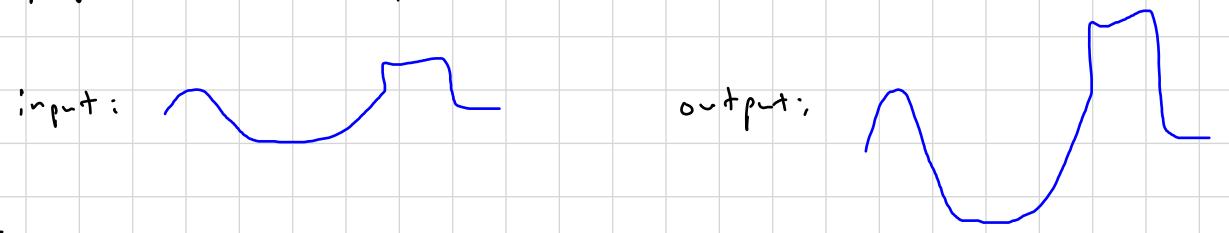


Common-Source MOSFET Amplifier

Linear Amplifier: magnifies input signal with output signal of larger magnitude but directly proportional to input; hence "linear"





current/voltage notations:

- i_D, v_{GS} — Total instantaneous values (at a specific instance of time)
- I_D, V_{GS} — DC values
- i_d, v_{gs} — Instantaneous AC values
- I_d, V_{gs} — Phasor values (we will not use these, just replace with the instantaneous ac values instead)

"small signal": able to linearize the ac equivalent circuit

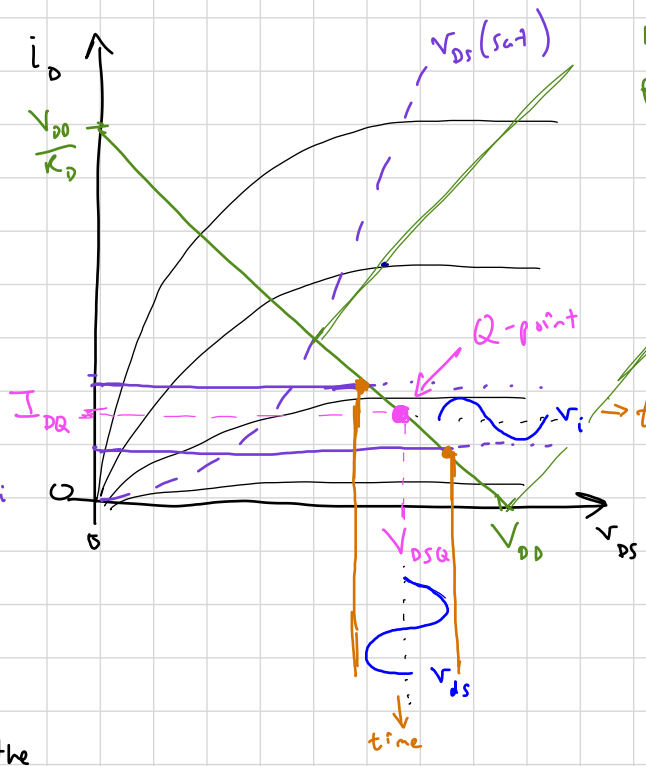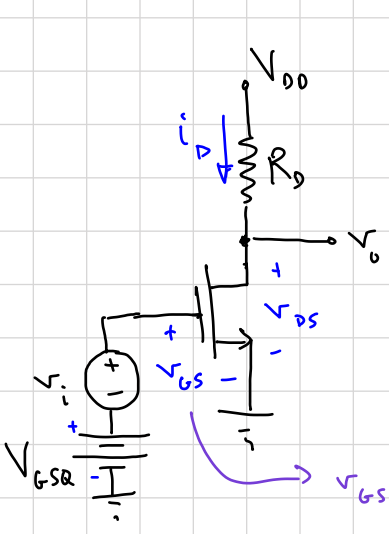Simple NMOS Common-Source Circuit with ac signal in series



must operate within the saturation on this part of the load line, otherwise will not be linear amplification!

$$v_{GS} = V_{GSQ} + v_i = V_{GSQ} + v_{gs}$$

$$i_D = K_n (v_{GS} - V_{TN})^2$$

$$i_D = K_n ((V_{GSQ} - V_{TN}) + v_{gs})^2$$

OR

$$i_D = K_n (V_{GSQ} - V_{TN})^2 + 2K_n (V_{GSQ} - V_{TN}) v_{gs} + K_n v_{gs}^2$$

I_{DQ} i_d

transconductance relates the small-signal i_d and v_{gs} :

$$\star g_m = \frac{i_d}{v_{gs}} = 2K_n (V_{GSQ} - V_{TN}) = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS} = V_{GSQ}}$$

→ represents the gain of the MOSFET

$$\star g_m = 2 \sqrt{K_n I_{DQ}}$$

condition must be satisfied to be a small-signal linear amplifier

produces distortion in amplification
So: $v_{gs} \ll 2(V_{GSQ} - V_{TN})$ \star


∴ neglect this term and get:

$$i_D = I_{DQ} + i_d$$

$$v_o = v_{DS} = V_{DD} - i_D R_D$$

$\star \Rightarrow$ Part of being a linear circuit is that we can analyze the ac & dc parts separately and then add!

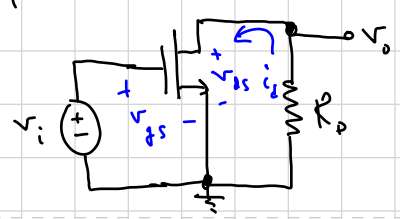→ AC equivalent circuit: set DC sources to zero:




$$v_{DS} = -i_d R_D$$

$$i_d = g_m v_{gs}$$


$$v_{gs} = v_i$$

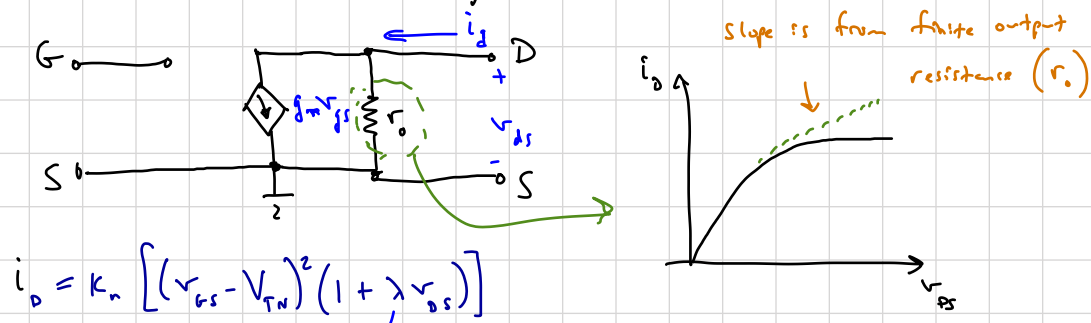→ one step further for ac equiv. circuit is to include the small-signal equiv. circuit for the MOSFET
(assuming low frequency)



$$r_o = \left(\frac{\partial i_D}{\partial V_{DS}} \right)^{-1} \bigg|_{V_{GS} = V_{GSD} = \text{constant}} = [\lambda I_{DQ}]^{-1}$$

Bringing these together:

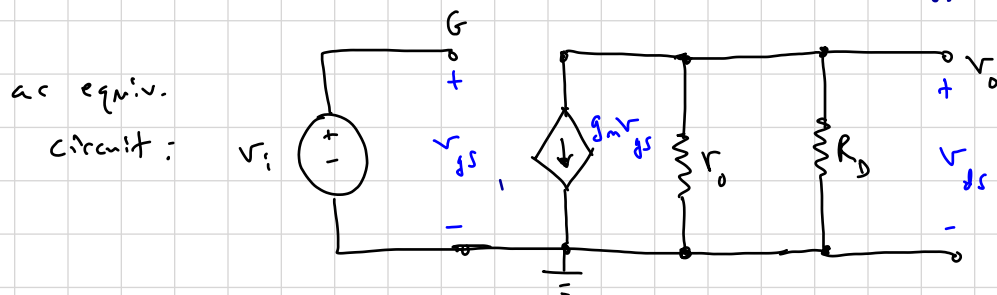



Small-signal voltage gain:

$$A_v = \frac{V_o}{V_i} = -g_m (r_o \parallel R_D)$$

$$\frac{r_o R_D}{r_o + R_D}$$

Look at steps in
book on
p. 594
(E-book)

Common-Source Amplifier

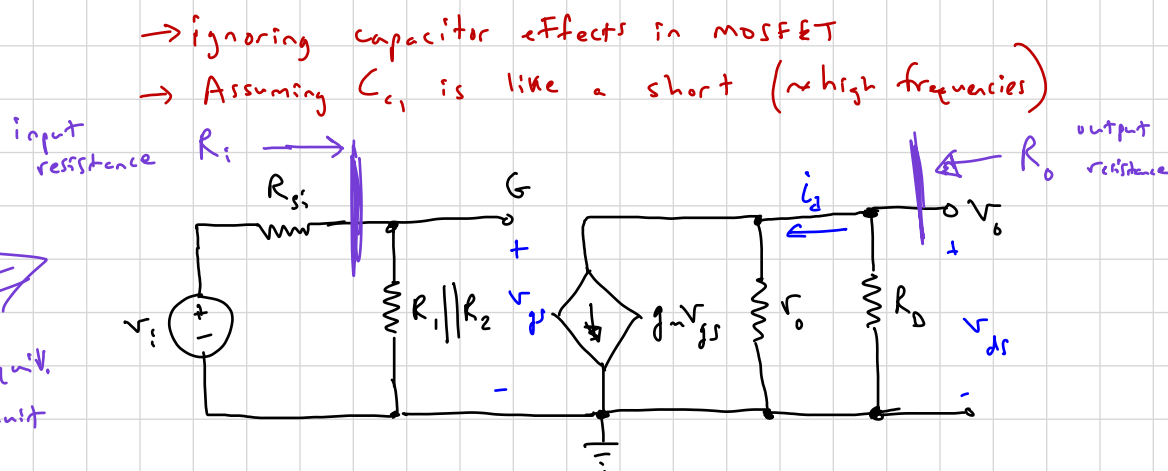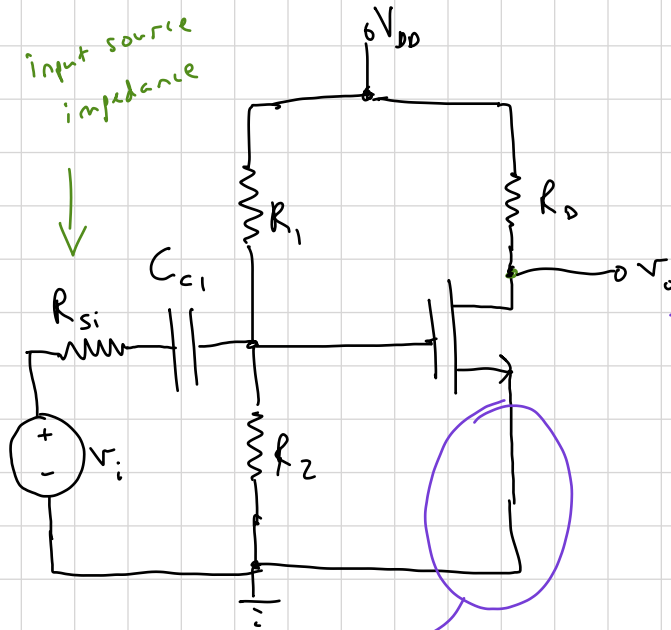

Find R_o by setting $V_i = 0$, $V_{GS} = 0$: $R_o = R_D \parallel r_o$

$$V_o = -g_m V_{GS} (r_o \parallel R_D), \quad V_{GS} = \left(\frac{R_i}{R_i + R_{Si}} \right) V_i$$

$\rightarrow R_{Si} \ll R_i$

$$\therefore A_v = \frac{V_o}{V_i} = -g_m (r_o \parallel R_D) \left(\frac{R_i}{R_i + R_{Si}} \right)$$

Options: ① Add source resistor (R_S)

to make Q-point more consistent
from transistor to transistor

→ loose some A_v

→ more stable Q-point

② Add bypass capacitor and constant current source

→ lessen A_v loss

→ further stabilize Q-point

→ increased complexity